



North South University

Department of Electrical & Computer Engineering

7 segment Display project CSE231


Project Report

Course name: CSE-231 (Digital Logic Design Lab)

Student name: Tasnim Shahrin

ID: 2022025042

State diagram

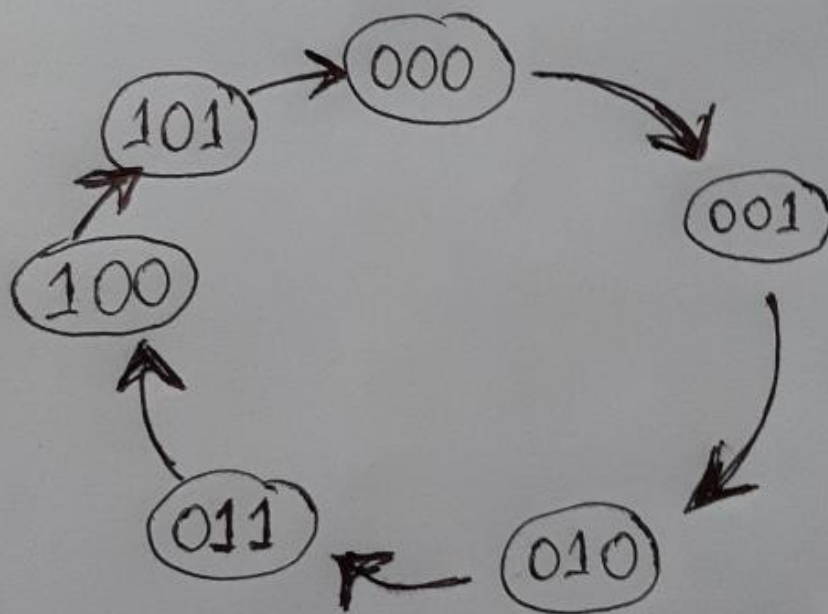

Excitation Table

Present State			Next State			JK flip-flop			T flip-flop			D flip-flop		
A_t	B_t	C_t	A_{t+1}	B_{t+1}	C_{t+1}	$J_A K_A$	$J_B K_B$	$J_C K_C$	T_A	T_B	T_C	D_A	D_B	D_C
0	0	0	0	0	1	0 x	0 x	1 x	0	0	1	0	0	1
1	0	1	0	1	0	0 x	1 x	x 1	0	1	1	0	1	0
2	0	1	0	1	1	0 x	x 0	1 x	0	0	1	0	1	1
3	0	1	1	0	0	1 x	x 1	x 1	1	1	1	1	0	0
4	1	0	1	0	1	x 0	0 x	1 x	0	0	1	1	0	1
5	1	0	0	0	0	1 0	0 x	x 1	1	0	1	0	0	0
6	1	1	0	x	x	x x	x x	x x	x	x	x	x	x	x
7	1	1	1	x	x	x x	x x	x x	x	x	x	x	x	x

K map

K map (JK flip-flop)

J_A:

A_t \ $B_t C_t$	00	01	11	10
0	0	0	1	0
1	X	X	X	X

$$J_A = B_t C_t$$

K_A:

A_t \ $B_t C_t$	00	01	11	10
0	X	X	X	X
1	0	1	X	X

$$K_A = C_t$$

J_B:

A_t \ $B_t C_t$	00	01	11	10
0	0	1	X	X
1	0	0	X	X

$$J_B = \overline{A_t} C_t$$

K_B:

A_t \ $B_t C_t$	00	01	11	10
0	X	X	1	0
1	X	X	X	X

$$K_B = B_t C_t$$

J_c:

A _t \ B _t C _t	00	01	11	10
0	1	X	X	1
1	1	X	X	X

$J_c = 1$

K_c:

A _t \ B _t C _t	00	01	11	10
0	X	1	1	X
1	X	1	X	X

$K_c = 1$

T flip-flop (K-map)

T_A:

A _t \ B _t C _t	00	01	11	10
0	0	0	1	0
1	0	1	X	X

$T_A = B_t C_t + A_t C_t$

T_B :

A_t	$B_t C_t$			
	00	01	11	10
0	0	1	1	0
1	0	0	X	X

$$T_B = \bar{A}_t C_t$$

 T_C :

A_t	$B_t C_t$			
	00	01	11	10
0	1	1	1	1
1	1	1	X	X

$$T_C = 1$$

D flip-flop (K-map) D_A :

A_t	$B_t C_t$			
	00	01	11	10
0	0	0	1	0
1	1	0	X	X

$$D_A = A_t \bar{C}_t + B_t C_t$$

 D_B :

A_t	$B_t C_t$			
	00	01	11	10
0	0	1	0	1
1	0	0	X	X

$$D_B = \bar{A}_t \bar{B}_t C_t + B_t \bar{C}_t$$

D_c :


A_t \ $B+C_t$	00	01	11	10
0	1	0	0	1
1	1	0	X	X


$$D_c = \overline{C_t}$$


1	1	1	1
X	X	1	1

D flip-flop (K-map)


A_t \ $B+C_t$	00	01	11	10
0	0	1	0	0
1	X	X	0	1

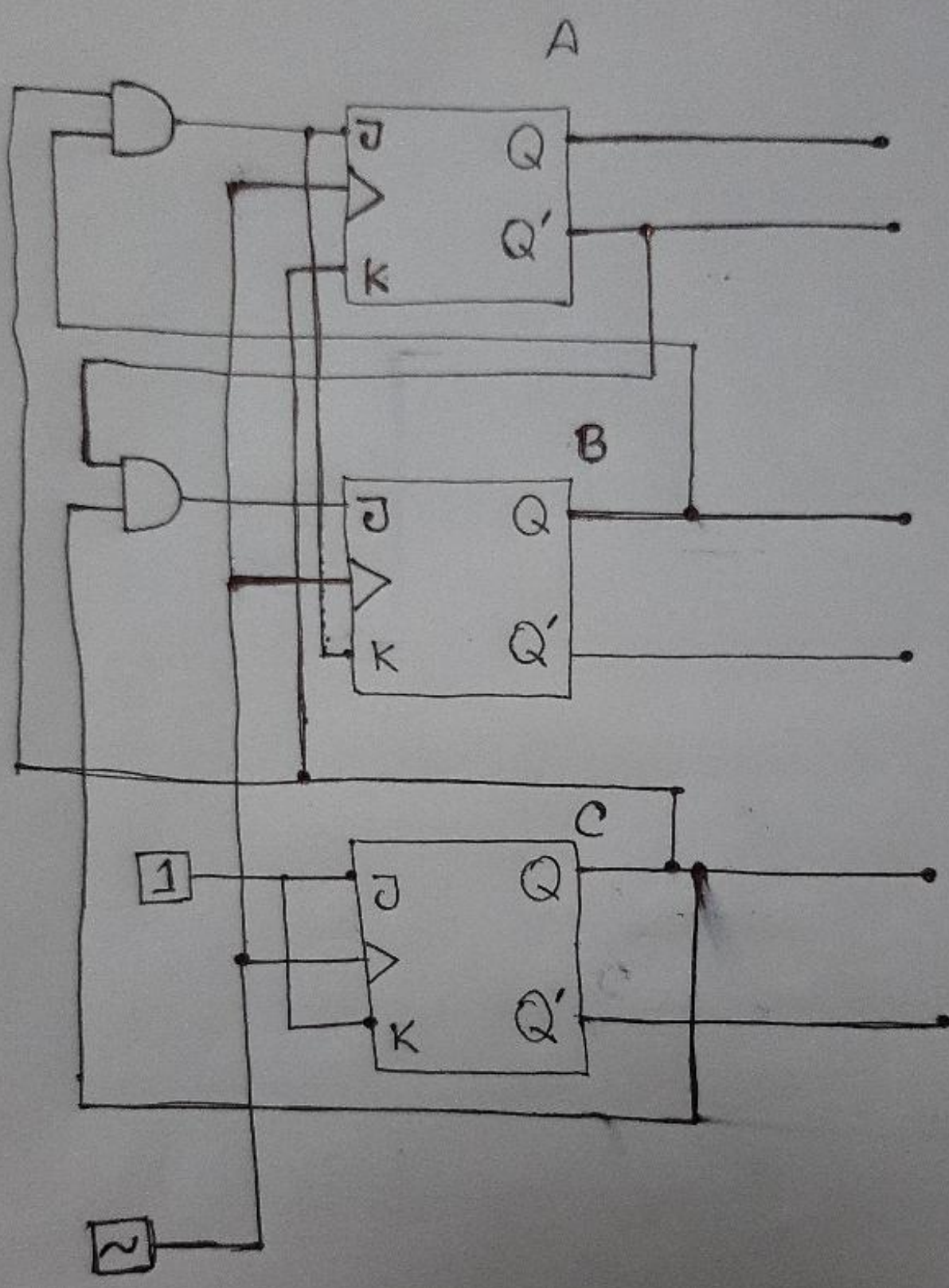

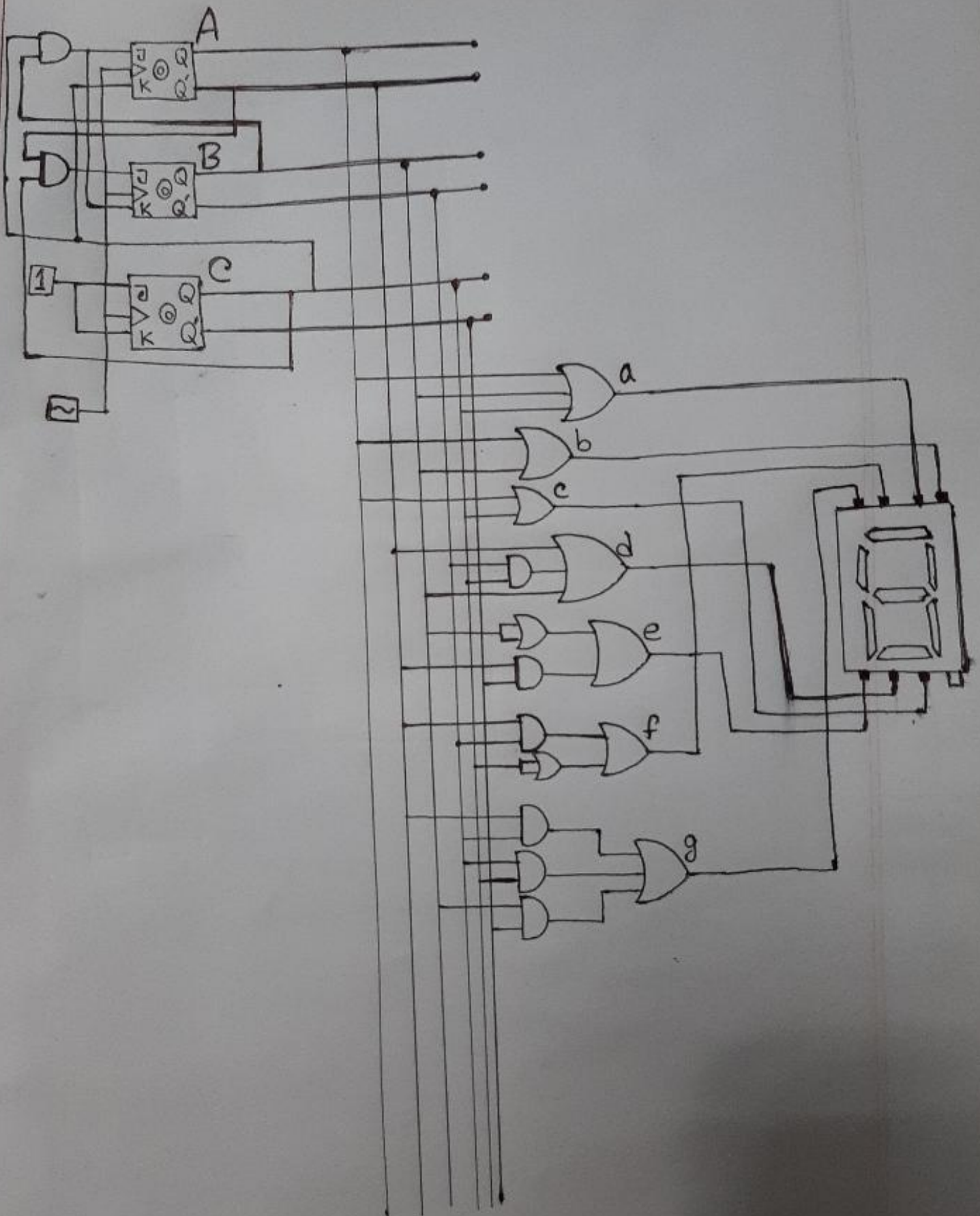

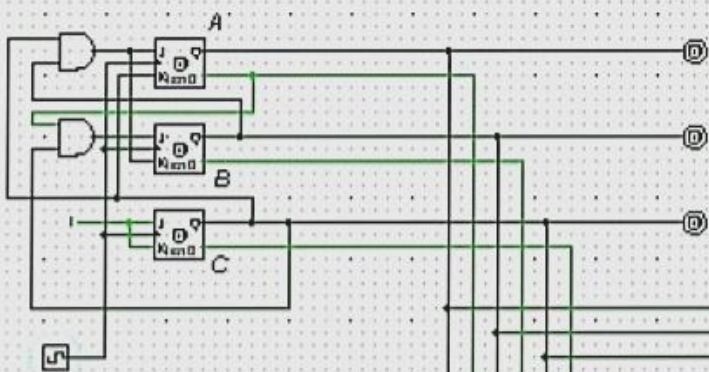


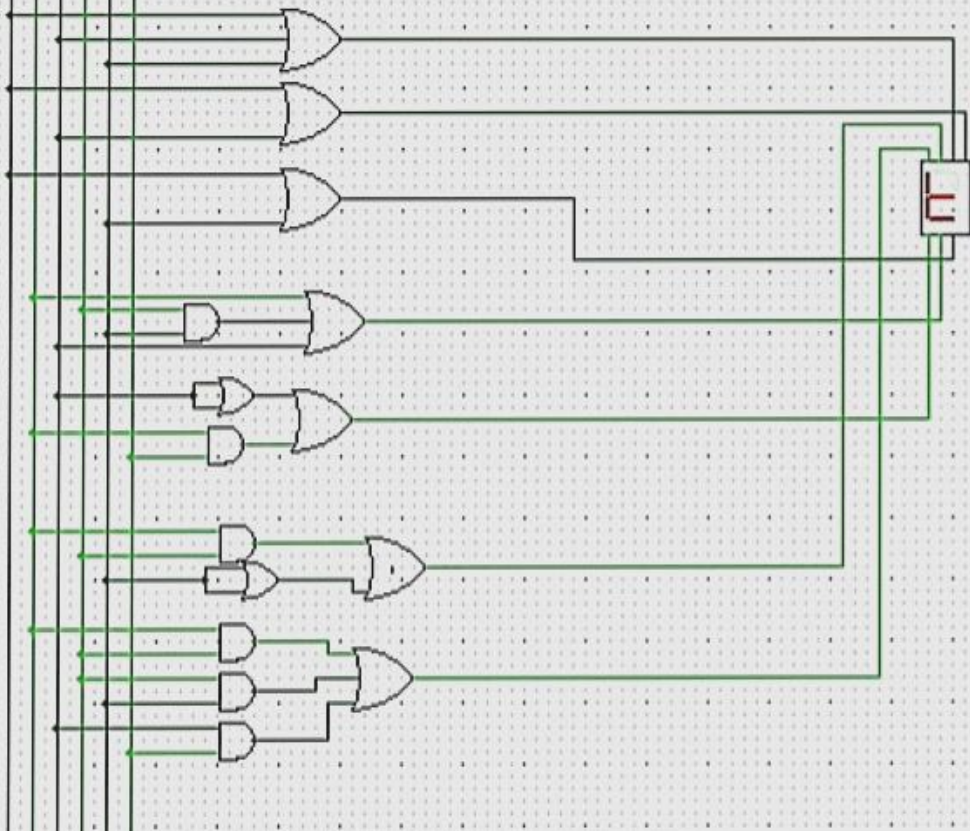
Sequential circuit
2022025042_Tasnim Shahrin



Sequential circuit


2022025042_Tasnim Shahrin

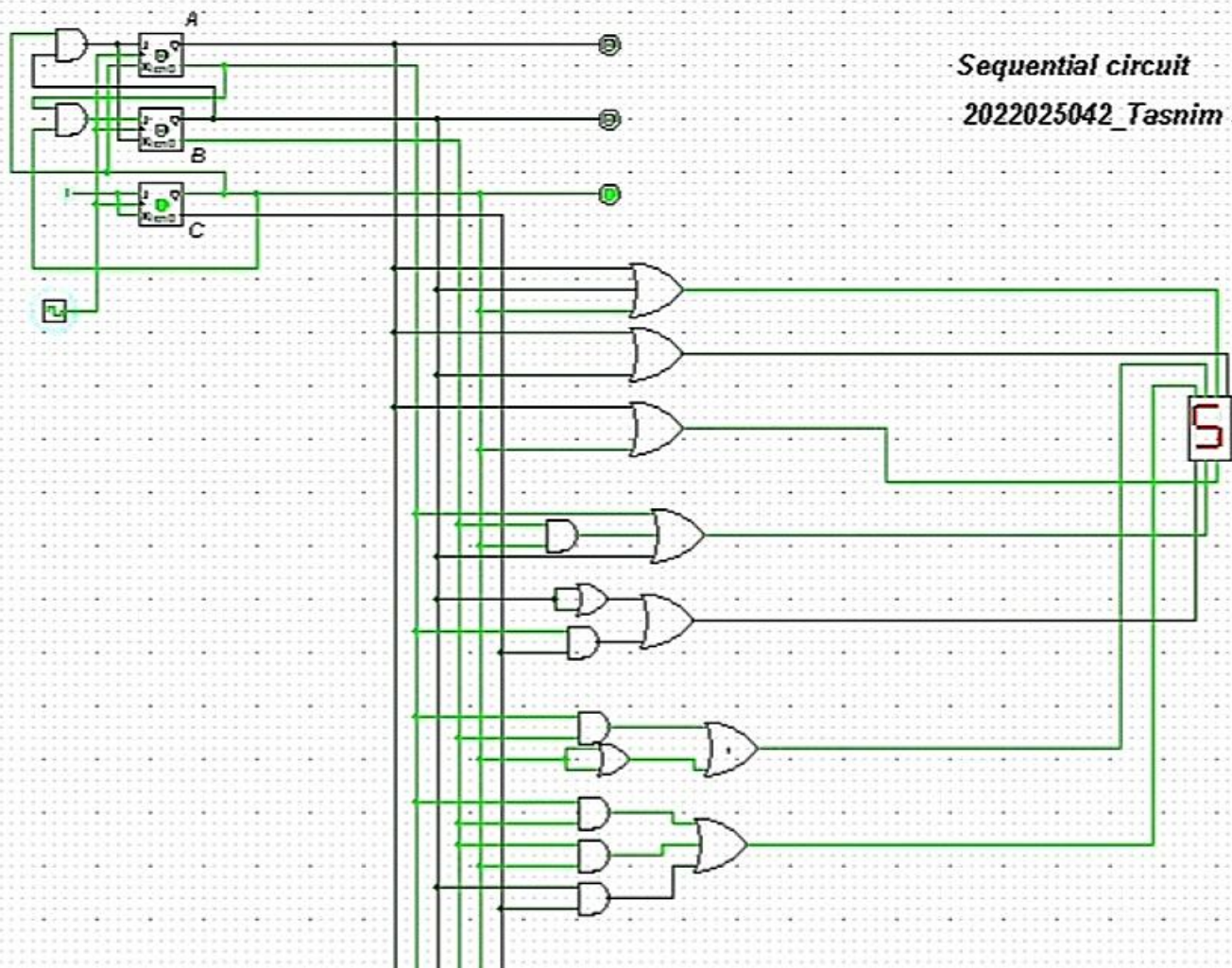


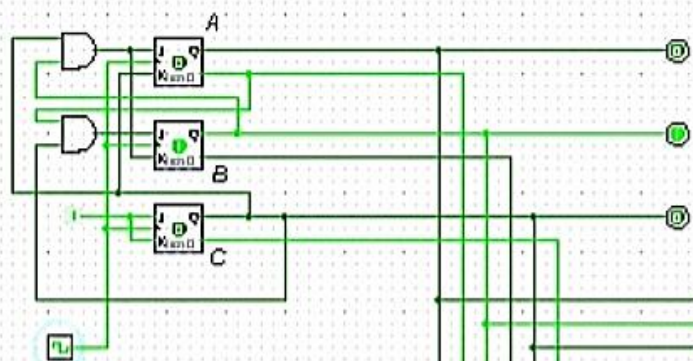

Sequential circuit

2022025042_Tashim Shahrin

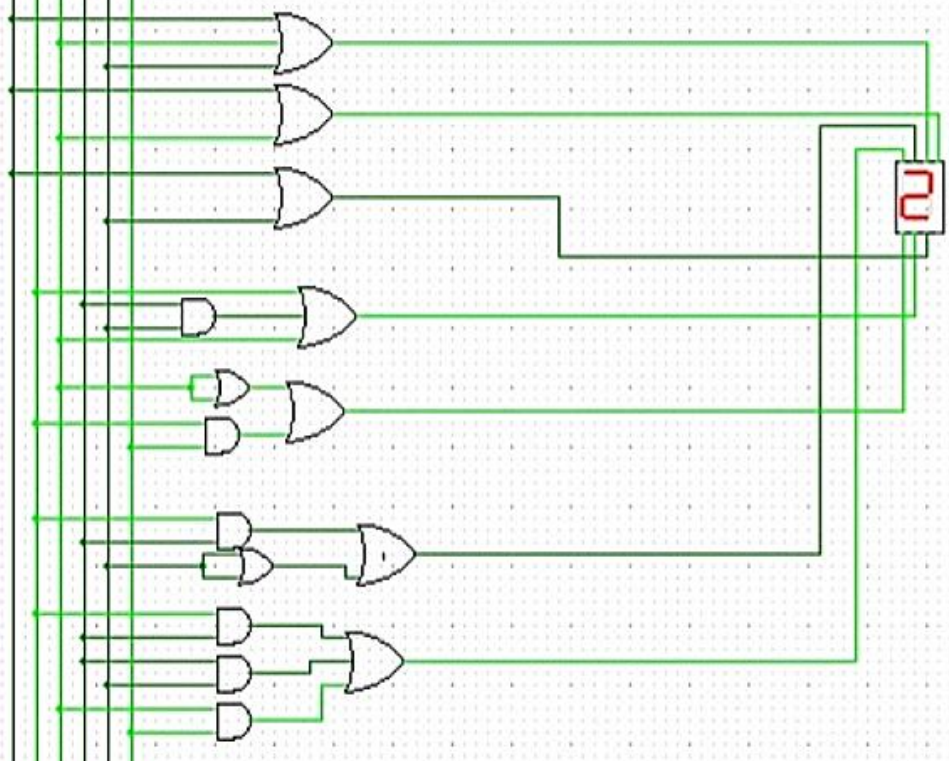

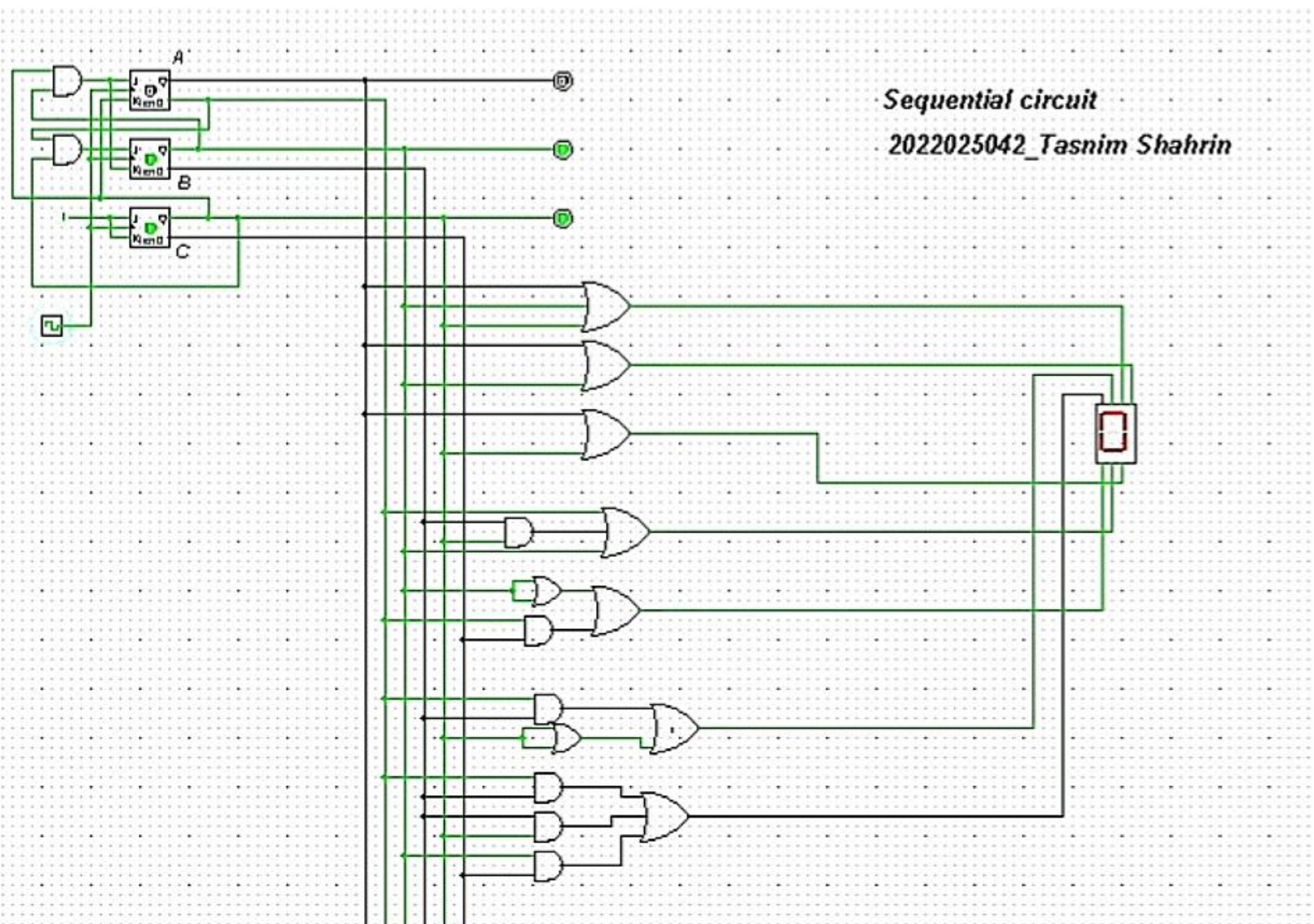


Sequential circuit

2022025042_Tasnim Shahrin

Sequential circuit

2022025042_Tasnim Shahrin

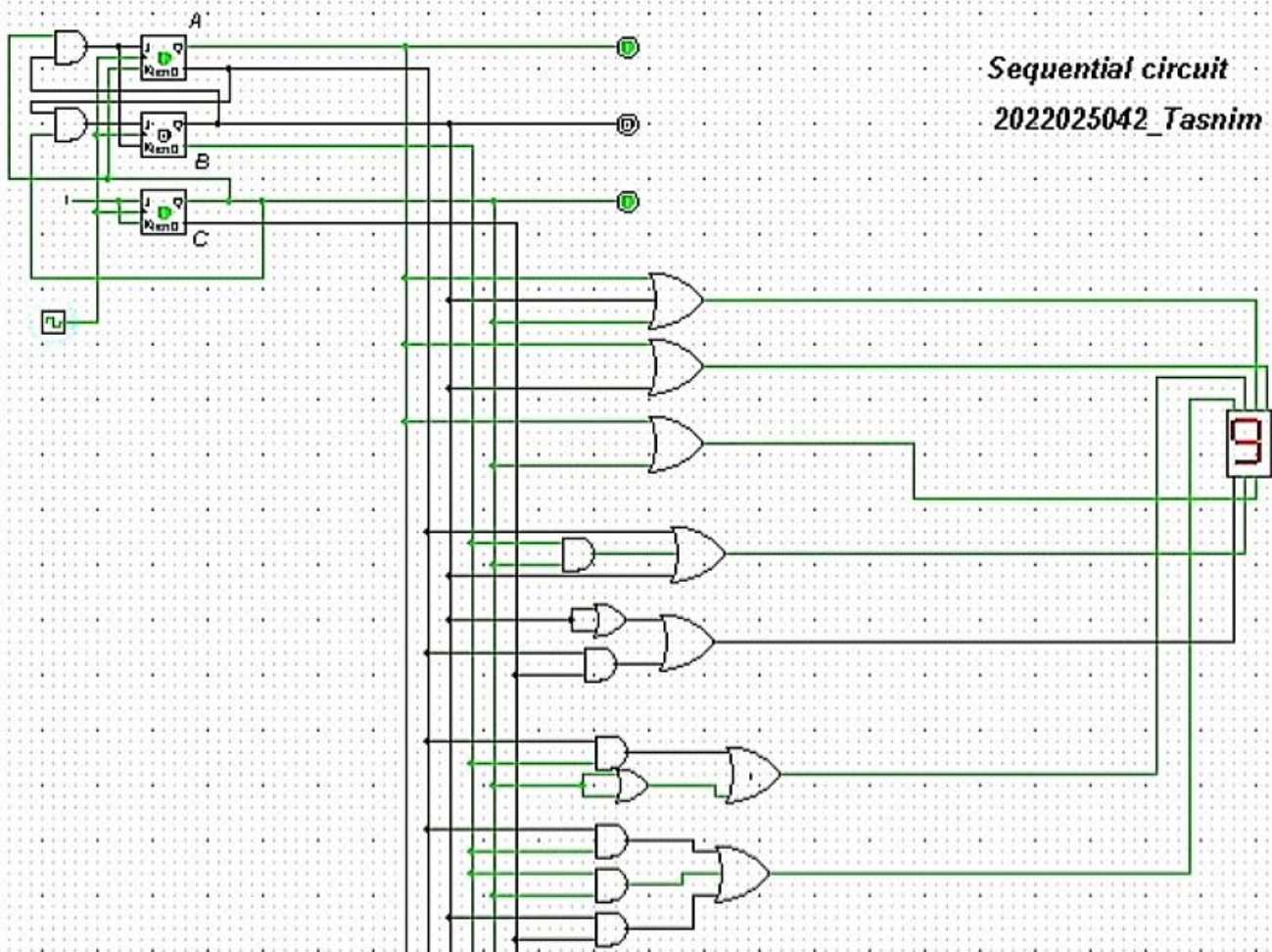

Cost analysis

Sequential circuit with combinational circuit :

Equipment list :

Component name	Quantity	Rate	Amount
Bread board	2	90/=	180/=
Wires	60	2/=	120/=
Dual JK flip-flop	3	20.9/=	62.7/=
7 Segment Display	1	22.67/= 9.85/=	22.67/= 9.85/=
IC 4075 (3 in OR)	1	22.67/=	22.67/=
IC 7432 (2 in OR)	2	27.59/=	55.18/=
IC 7408 (2 in AND)	2	23.59/=	47.18/=
IC 7404 (Hex Inverter NOT)	1	25.59/=	25.59/=
1N 4148 High Speed Switch	1	1.9/=	1.9/=

Total = 525.07/=

Discussion :

In this project we I made 7-segment display to display "TS2079".

At first we I made the truth table. By using the truth table we I got SOP and POS equations. I draw the circuits of SOP and POS in the generalized and simplified form.

I also did K-maps for SOP and POS. By the K-maps we got the simplified form. The simplified form ~~is~~ made the circuit quite simple and short.

After that we I use the 3 to 8 line decoder, and 4:1 MUX. and use the same truth table to display 7-segment "TS2079".

I also draw and simulate the simplification form of SOP and POS by using NAND and NOR gates.

I draw and simulate the sequential circuit with combinational circuit. I use JK flip-flop to make the input automated.

Typically for a standard red colored 7-segment display, Each LED segment can draw about 15 mA to illuminated correctly, So on a 5V digital logic circuit, the value of the current limiting resistor would be about $200\Omega (5V - 2V) / 15$ or 220Ω to the nearest higher preferred value.

So, to understand how the segments of the display are connected to a 220Ω current limiting resistor considers the circuit below.

Conclusion:

This project was good opportunity for all of us to learn how the system works and learn the theory as well. We also faced a lot of problems which taught us what kind of problems can be faced while building a 7-segment display. We had problems mostly with lack of knowledge on how to build everything but with a great deal of time spent on it together we figured it out eventually.