

North South University

Department of Electrical & Computer Engineering

7 segment Display project CSE231

Project Report

Course name: CSE-231 (Digital Logic Design Lab)

Student name: Tasnim Shahrin

ID: 2022025042

7-Segment Display

2022025042

Tasnim Shahnin (Sec→06)

Abstract:

In this project I made 7-segment display to display "TS2079". At first I made the truth table for the give display values.

Then I used the SOP and POS equation in generalized form. After that I found out the Simplified form of SOP and POS by using K-maps.

Finally I was able to make a circuit in logisim and also verify it.

Introduction:

In this project I ~~had~~ made a circuit in logisim. I used 3-input and got the output. $[2^3 = 8]$.

We give $t = 000$, $S = 001$, $2 = 010$, $0 = 011$, $7 = 100$, $9 = 101$.

I use basic gates to make it and one 7-segment display.

forward 809 bin 909 to most buildings

Object:

Our objective for this project is to build a 7-segment display that will display the following "1S2079"

There are mainly 2 parts to this project first is combinational part where we will have to give inputs manually and the second part is sequential part where we no longer have to give input ourselves and it will automatically display our desire output.

We were asked to show the combinational part where

we no longer have to give input manually. The input will be given by a 3-bit counter, with the

Theory:

7-segment Display

The 7-segment display, also written as "Seven Segment display", consists of seven LEDs (hence its name) arranged in a rectangular fashion as shown.

Each of the seven LEDs is called a segment forms part of a numerical digit (both decimal and Hex) to be displayed. An additional 8th LED is sometimes used within the same package thus allowing the indication of a decimal point, (DP) when two or more 7-segment displays are connected together to display numbers greater than ten. Each one of the seven LEDs in this display is given a positional segment with one of its connection pins being brought straight out of the rectangular plastic package. These individually LED

pins are labeled from 1 through 20 representing each individual LED. The other LED pins are connected together and wired to form a common pin.

Truth table:

	BCD (Inputs)			7-segment Display (Outputs)						
	A	B	C	a	b	c	d	e	f	g
E	0	0	0	0	0	0	1	1	1	1
5	0	0	1	1	0	1	1	0	1	1
2	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	1	1	0
7	1	0	0	1	1	1	1	0	0	0
9	1	0	1	1	1	1	1	1	0	1
	1	1	0	x	x	x	x	x	x	x
	1	1	1	x	x	x	x	x	x	x

Generalized Equation (SOP) :-

$$a = A'B'C + A'BC' + A'BC + AB'C' + AB'C$$

$$b = A'BC' + A'BC + AB'C' + AB'C$$

$$c = A'B'C + A'BC + AB'C' + AB'C$$

$$d = A'B'C' + A'B'C + A'BC' + A'BC + AB'C$$

$$e = A'B'C' + A'BC' + A'BC$$

$$f = A'B'C' + A'B'C + A'BC + AB'C$$

$$g = A'B'C' + A'B'C + A'BC' + AB'C$$

Generalized Equation (POS) :-

$$a = (A + B + C)$$

$$b = (A + B + C) \cdot (A + B + C')$$

$$c = (A + B + C) \cdot (A' + B' + C)$$

$$d = (A' + B + C)$$

$$e = (A + B + C') \cdot (A' + B' + C') \cdot (A + B' + C)$$

$$e = (A + B + C') \cdot (A' + B + C) \cdot (A' + B + C')$$

$$f = (A + B' + C) \cdot (A' + B + C)$$

$$g = (A + B' + C') \cdot (A' + B + C)$$

$$G + AB'G + ABG + G$$

$$G + AB'G + ABG + G$$

Simplified (SOP)

for a:

A \ BC₀

	00	01	11	10	
0	0	1	1	1	
1	1	1	X	X	

$$a = A + B + C$$

$$9 + A = 9$$

for b:

A\BC

	00	01	11	10
0	0	0	1	1
1	1	1	\times	\times

$$b = A + B$$

for C:

A \ BC		00	01	11	10
0	1	0	0	1	
1	0	0	0	X	X

$$(A+C) = C$$

for d:

A \ BC		00	01	11	10
0	0	0	0	0	
1	1	0	X	X	

$$(A'+B+C) = d$$

for e:

A \ BC		00	01	11	10
0	0	1	0	0	
1	1	1	X	X	

$$(A'+B) \cdot (B+C') = e$$

for f:

A\BC	00	01	11	10
0	0	0	0	1
1	1	0	x	x

$$f = (A+B'+C) \cdot (A'+B+C)$$

for g:

A\BC	00	01	11	10
0	0	0	1	0
1	1	0	x	x

$$g = (A+B'+C') \cdot (A'+B+C)$$

Simplified SOP:

$$\therefore a = A + B + C$$

$$b = A + B$$

$$c = A + C$$

$$d = A' + B'C + B$$

$$e = B + A'C'$$

$$f = A'B' + C$$

$$g = A'B' + B'C + BC'$$

Simplified (POS)

for a :

$A \setminus BC$

	00	01	11	10
0	1	0	X 0	0
1	0	0	X	X

$$(A+B+C) = a$$

for b :

$A \setminus BC$

	00	01	11	10
0	1	1	0	0
1	0	0	X	X

$$(A+B) = b$$

$$S = (B \cdot A) \cdot (B \cdot \bar{A})$$

for C:

A \ BC		00	01	11	10
0	1	0	0	1	1
1	0	0	0	X	X

$$(A+C) = C$$

for d:

A \ BC		00	01	11	10
0	0	0	0	0	0
1	1	0	X	X	0

$$(A' + B + C) = d$$

for e:

A \ BC		00	01	11	10
0	0	1	0	0	0
1	1	1	X	X	1

$$(A' + B) \cdot (B + C') = e$$

for f:

A\BC	00	01	11	10
0	0	0	0	1
1	1	0	x	x

$$f = (A+B'+C) \cdot (A'+B+C)$$

for g:

A\BC	00	01	11	10
0	0	0	1	0
1	1	0	x	x

$$g = (A+B'+C') \cdot (A'+B+C)$$

Simplified POS:

$$a = A + B + C$$

$$b = A + B$$

$$c = A + C$$




$$d = A' + B + C$$

$$e = (A' + B) \cdot (B + C')$$

$$f = (A + B' + C) \cdot (A' + B + C)$$

$$g = (A + B' + C') \cdot (A' + B + C)$$

Designed POS SOP with NAND gates

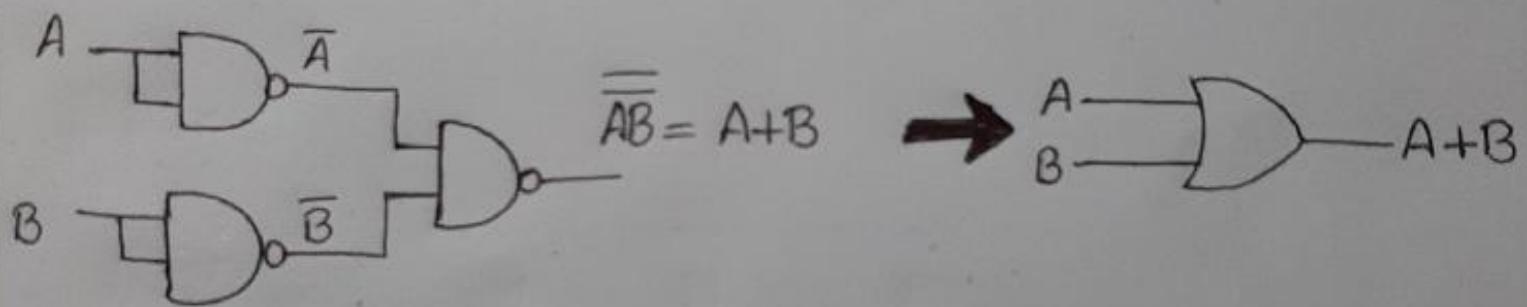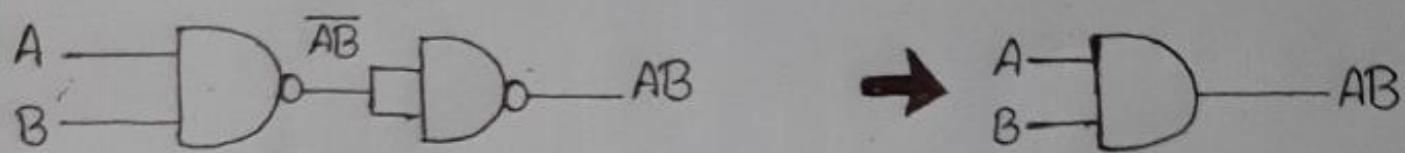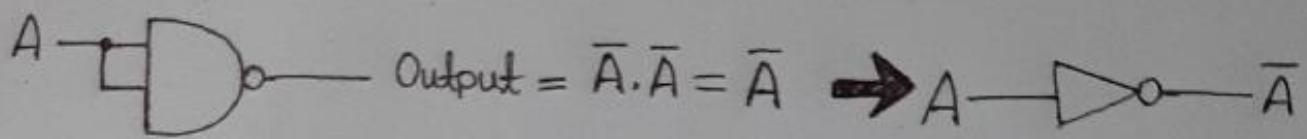

~~MUX~~ MUX 7 Segment Display

for a:

	I_0	I_1	I_2	I_3
\bar{C}	0	1	1	x
C	1	1	1	x
C	1	1	1	x

for b:

	I_0	I_1	I_2	I_3
\bar{C}	0	1	1	x
C	0	1	1	x
0	1	1	1	x

for c:

	I_0	I_1	I_2	I_3
\bar{C}	0	0	1	x
C	1	1	1	x
C	C	C	1	x

for d:

	I_0	I_1	I_2	I_3
\bar{C}	1	1	0	x
C	1	1	1	x
	1	1	C	x

for e:

	I_0	I_1	I_2	I_3
\bar{C}	1	1	0	x
C	0	1	0	x
	\bar{C}	1	0	x


for f:

	I_0	I_1	I_2	I_3
\bar{C}	1	0	0	x
C	1	1	1	x
	1	C	C	x

for g:


	I_0	I_1	I_2	I_3
\bar{C}	1	1	0	x
C	1	0	1	x
	1	\bar{C}	C	x


Generalized equation SOP

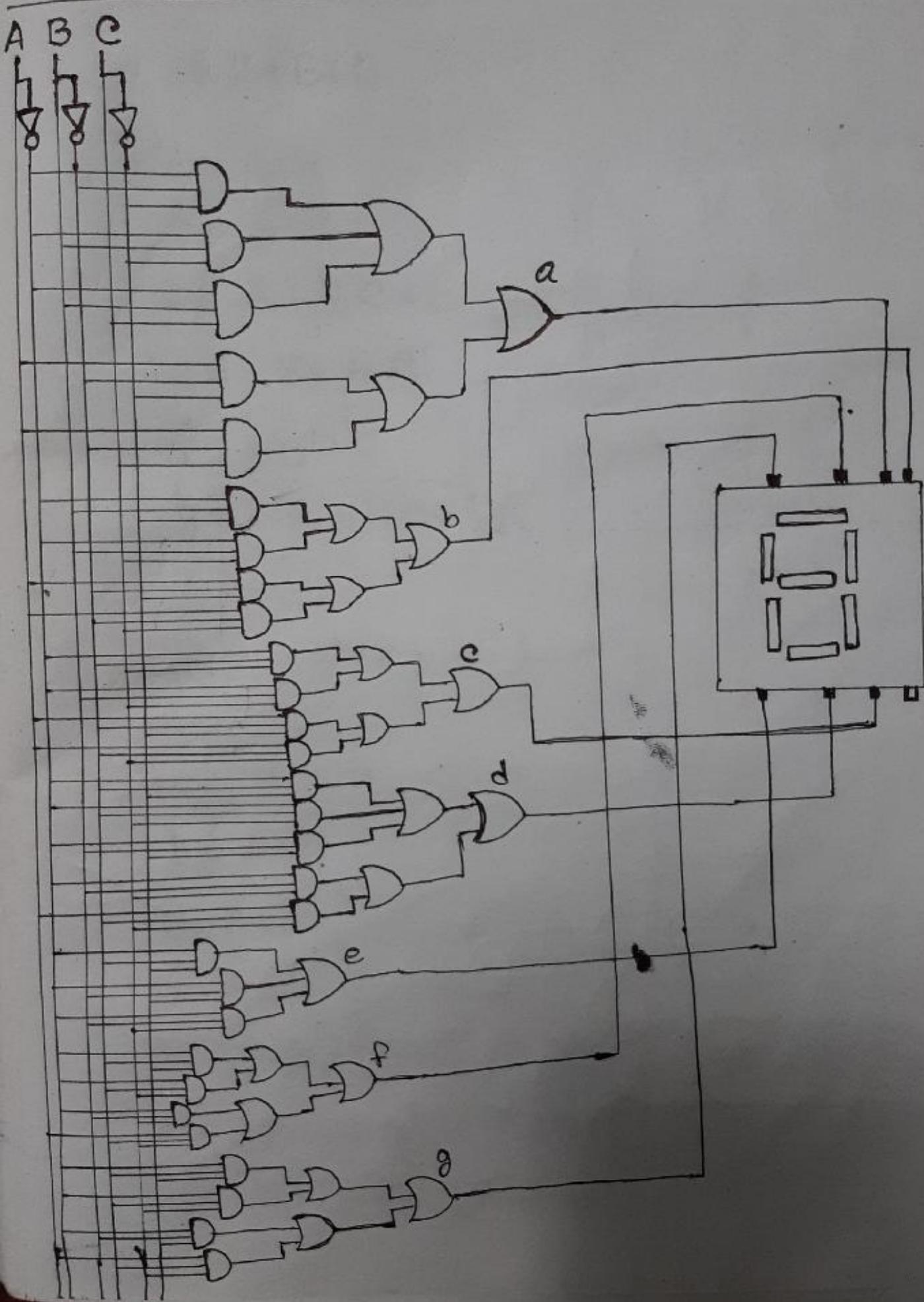


GENERALIZED SOP

2022025042_Tasnim Shahrin

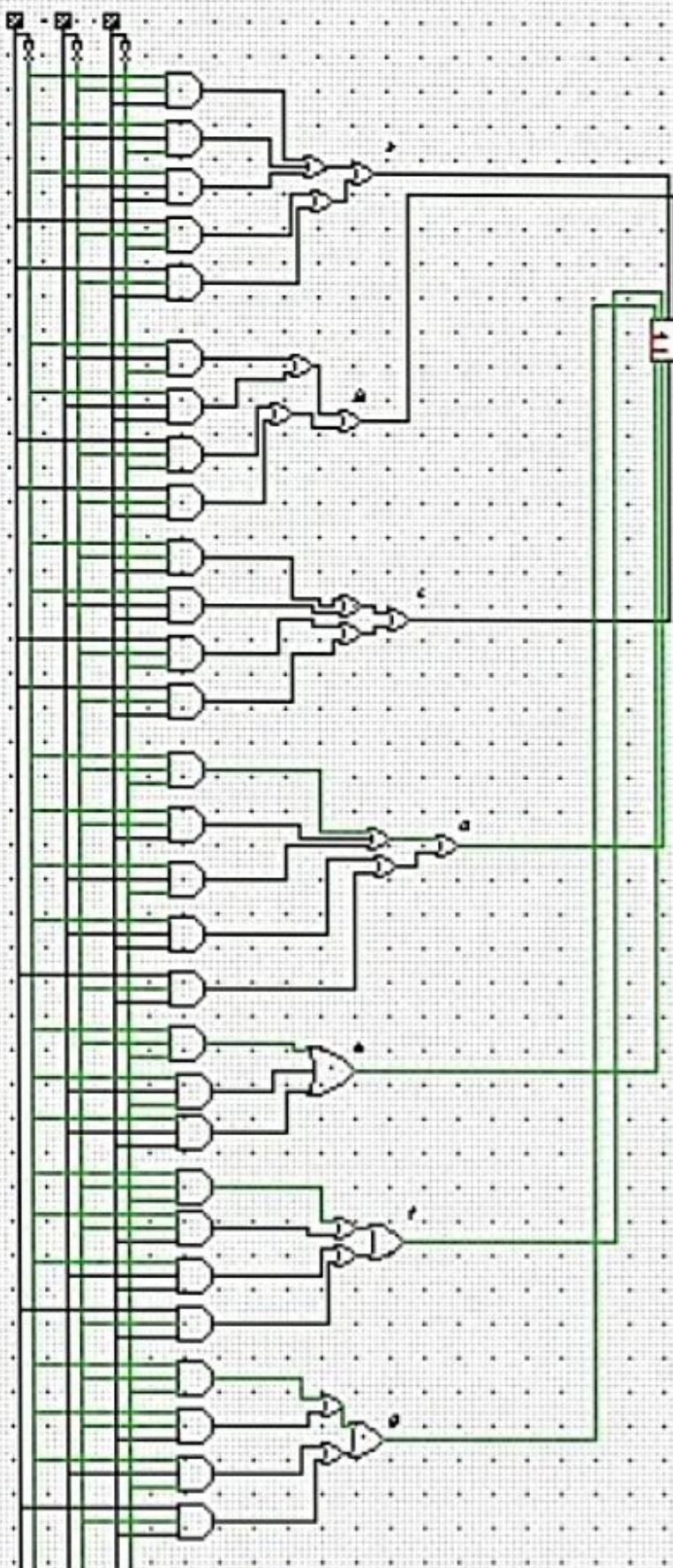


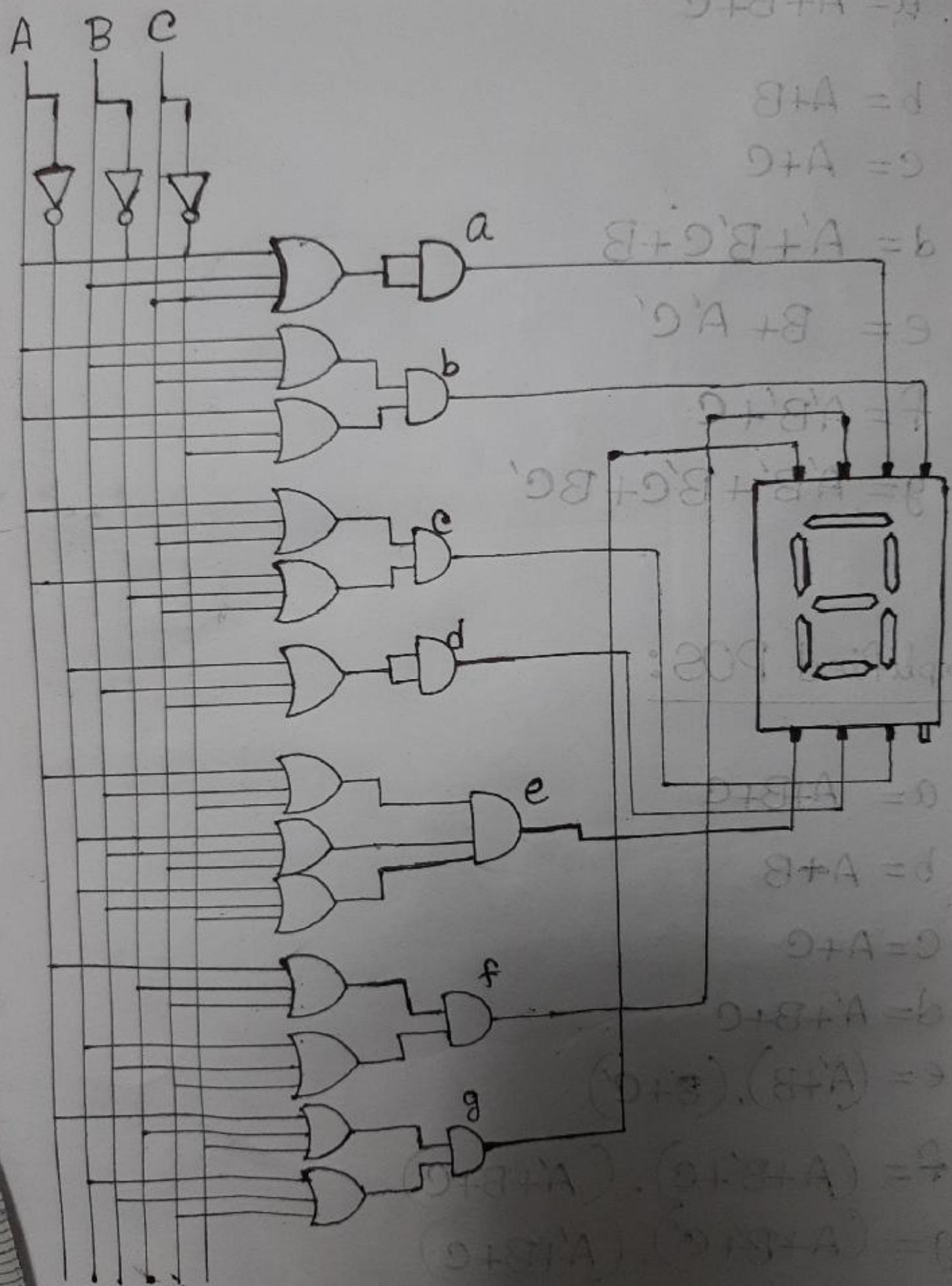

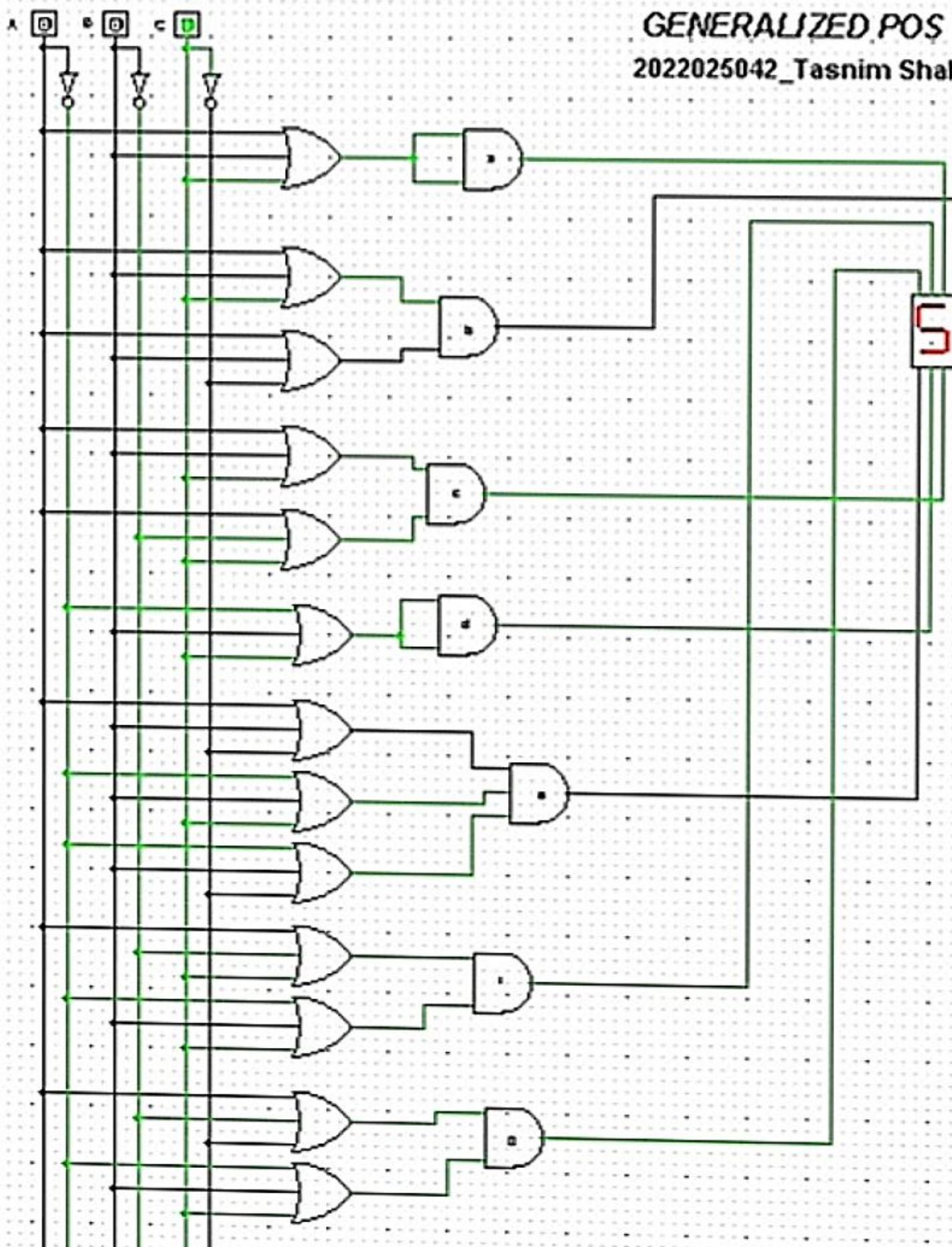
GENERALIZED POS
2022025042_Tasnim Shahrin




Simplified SOP

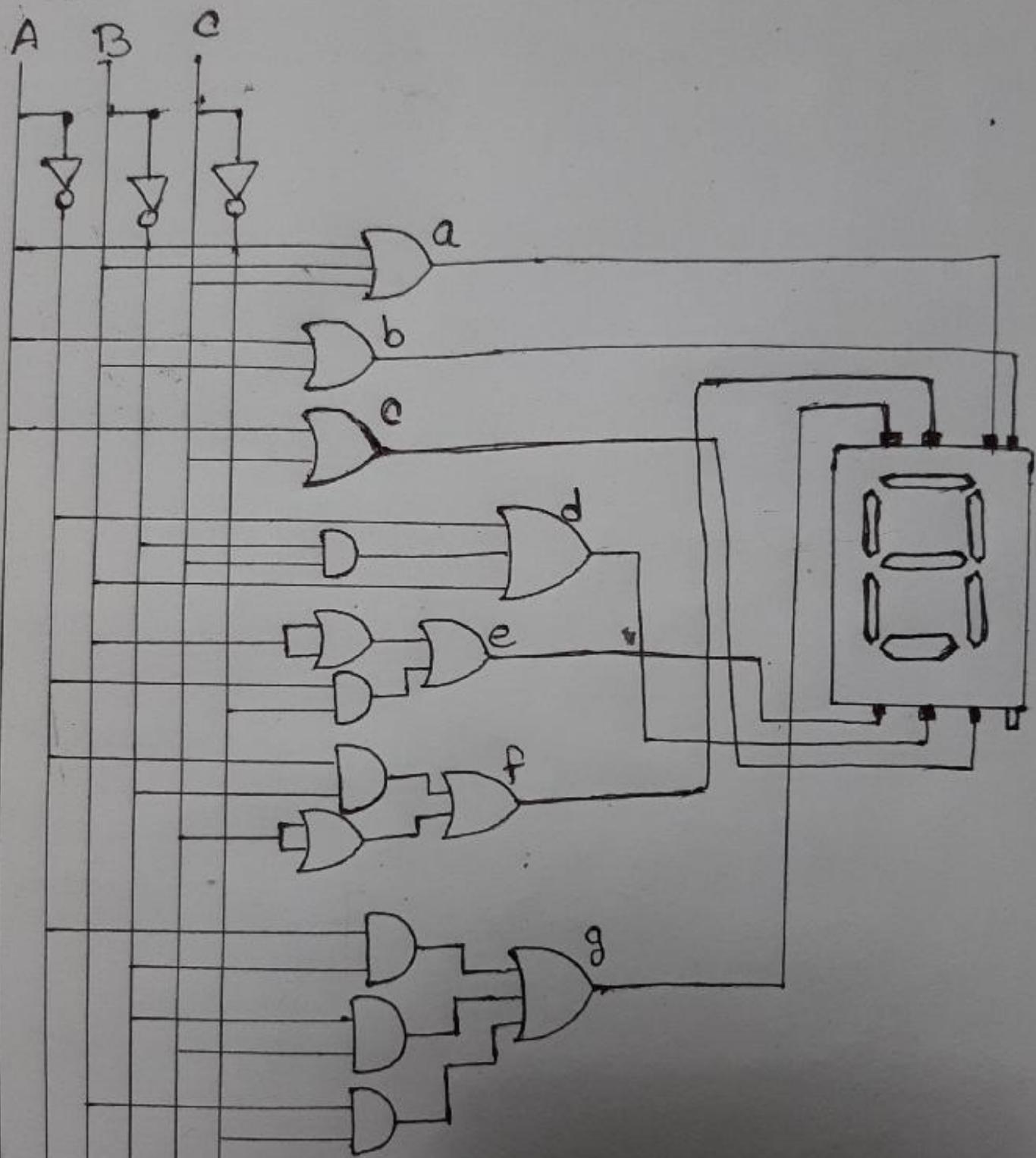


SIMPLIFIED SOP
2022025042_Tasnim Shahrin

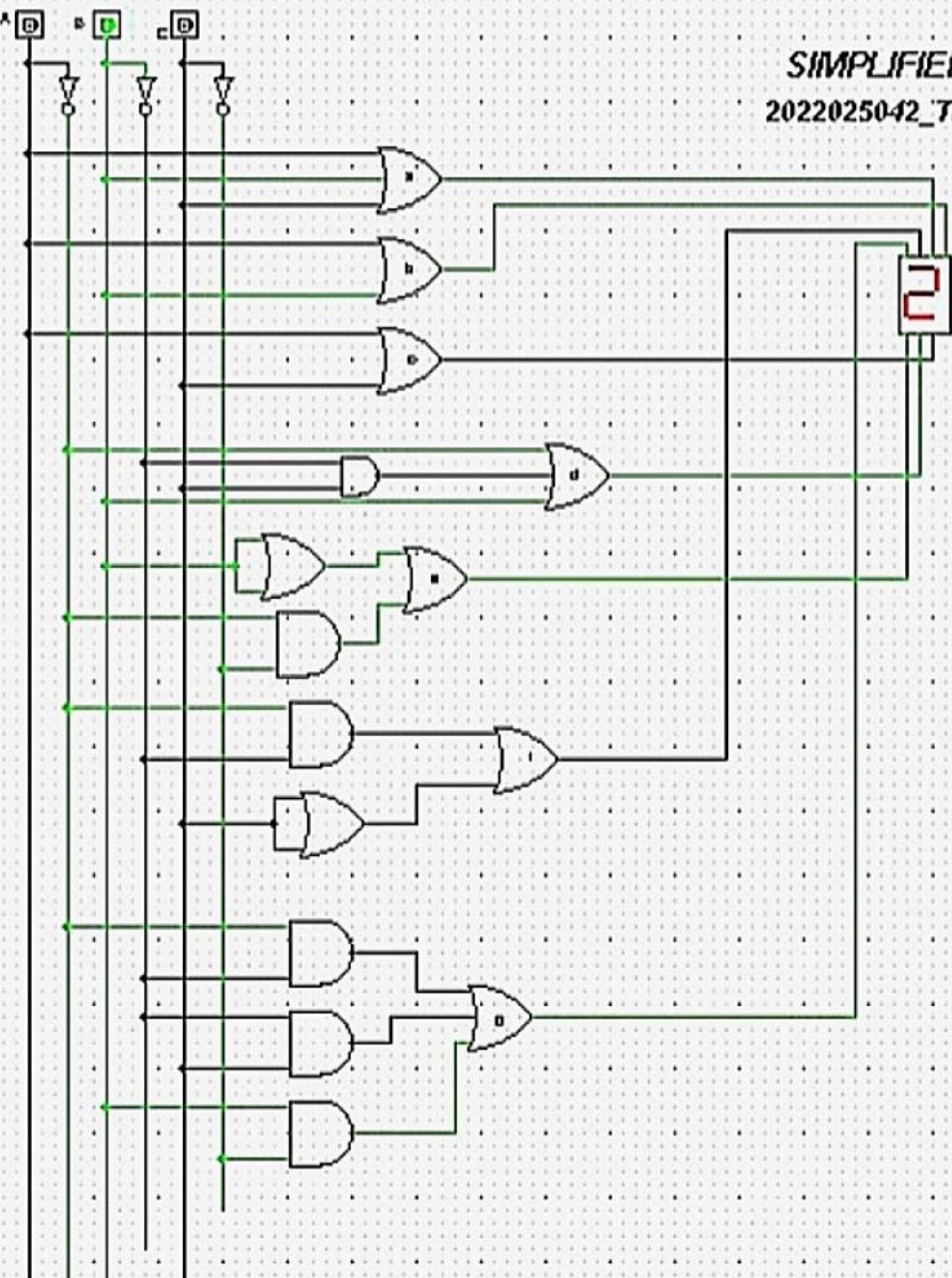



Simplified ~~SOP~~ POS

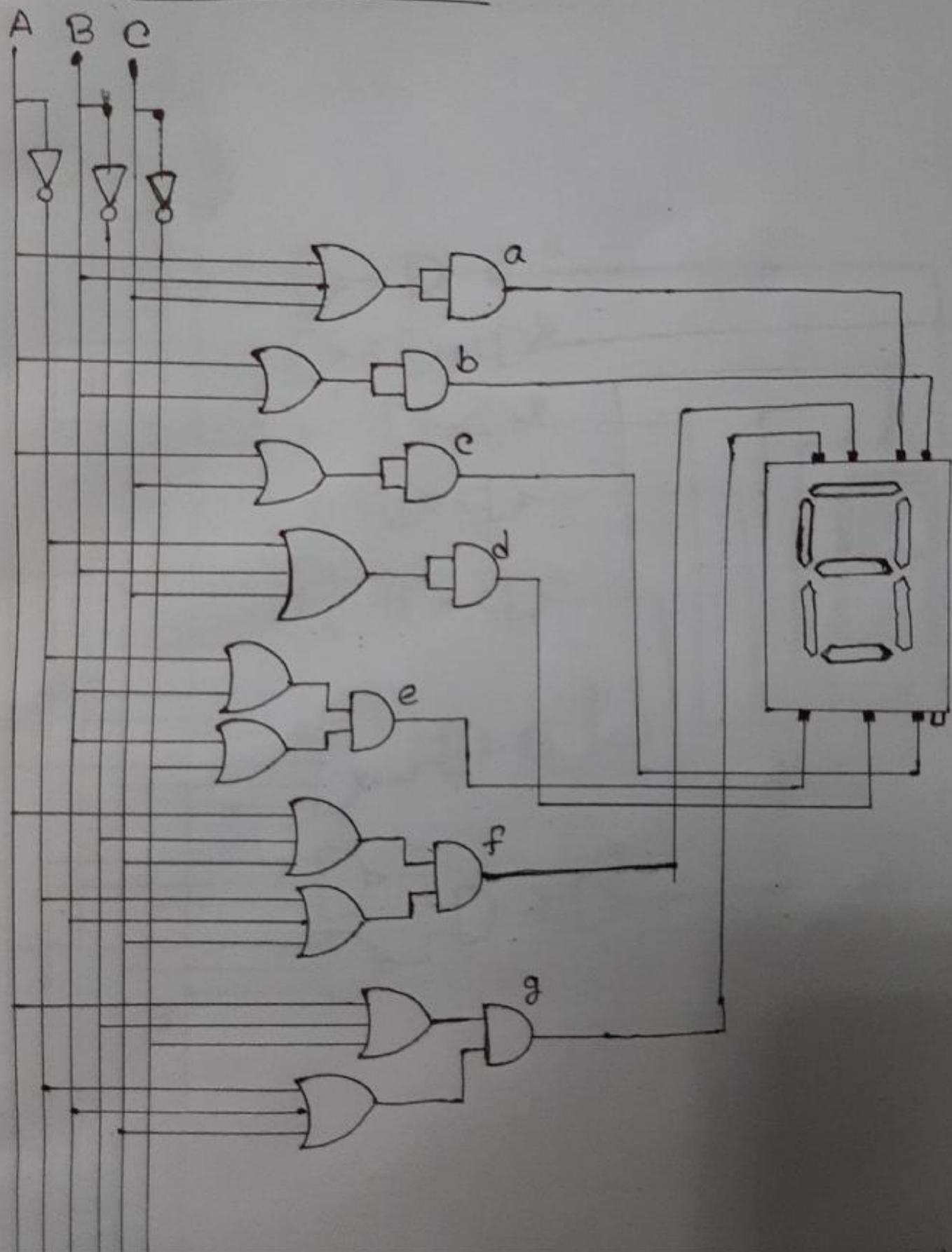

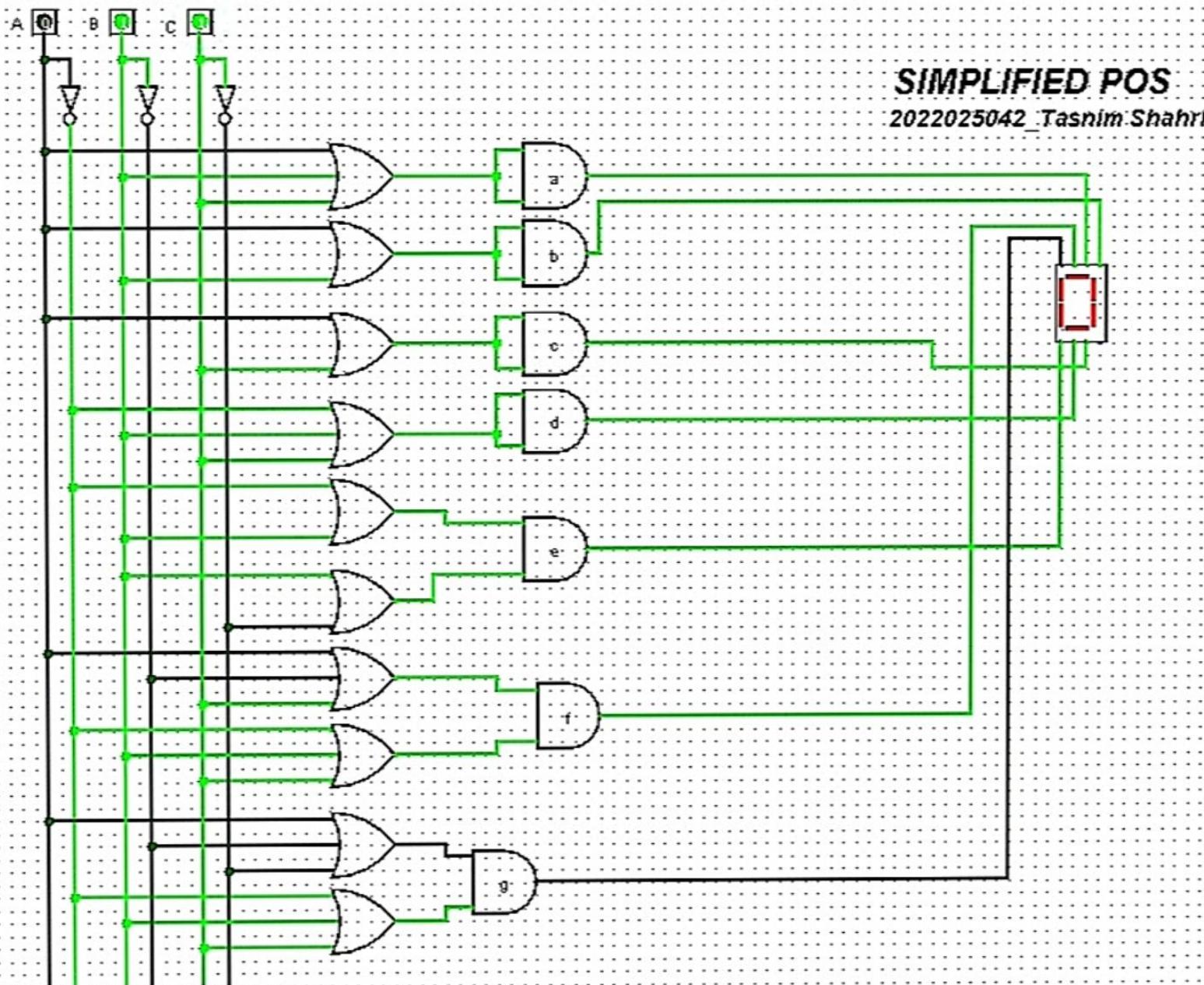


NAND gate POS

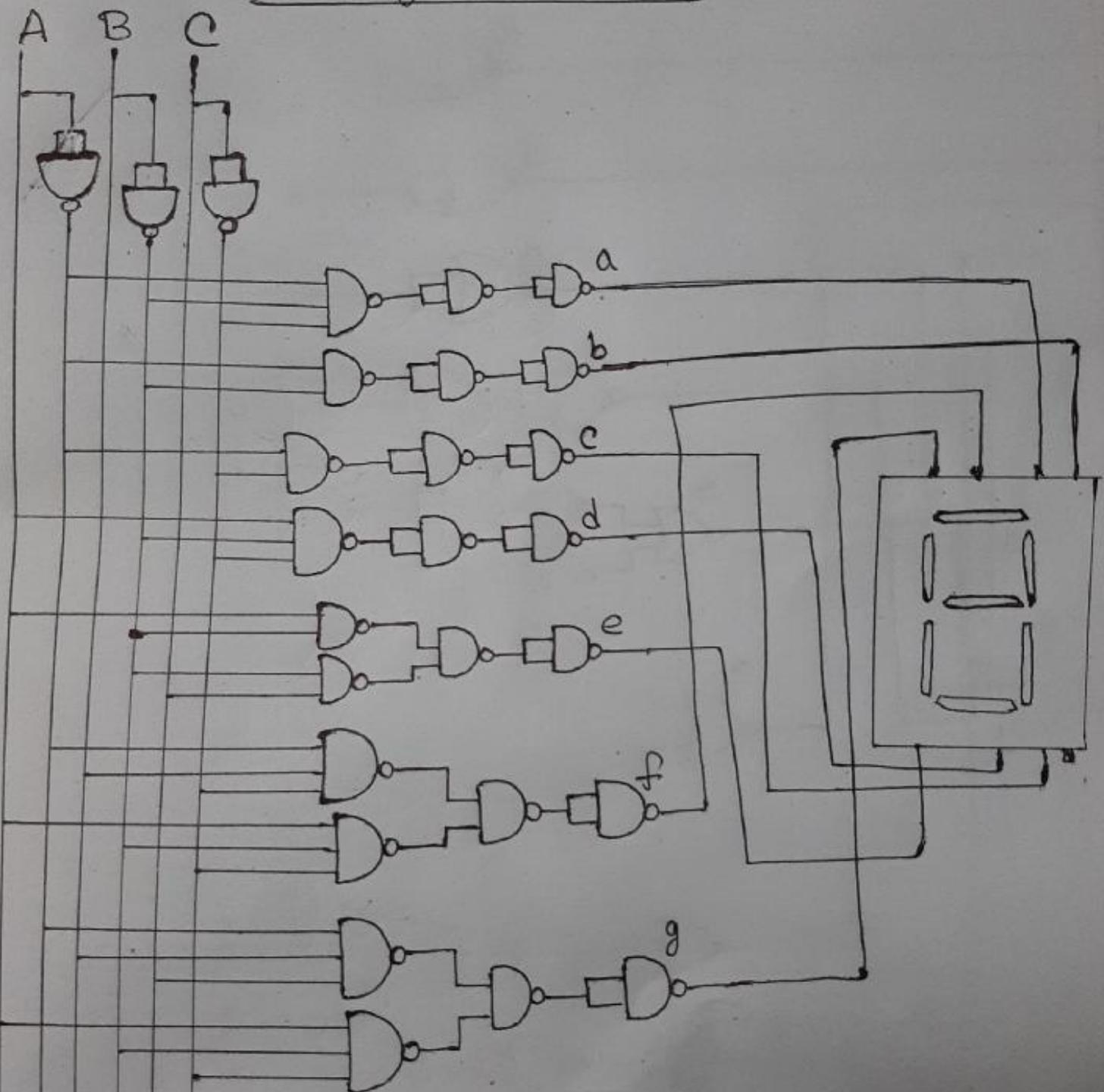

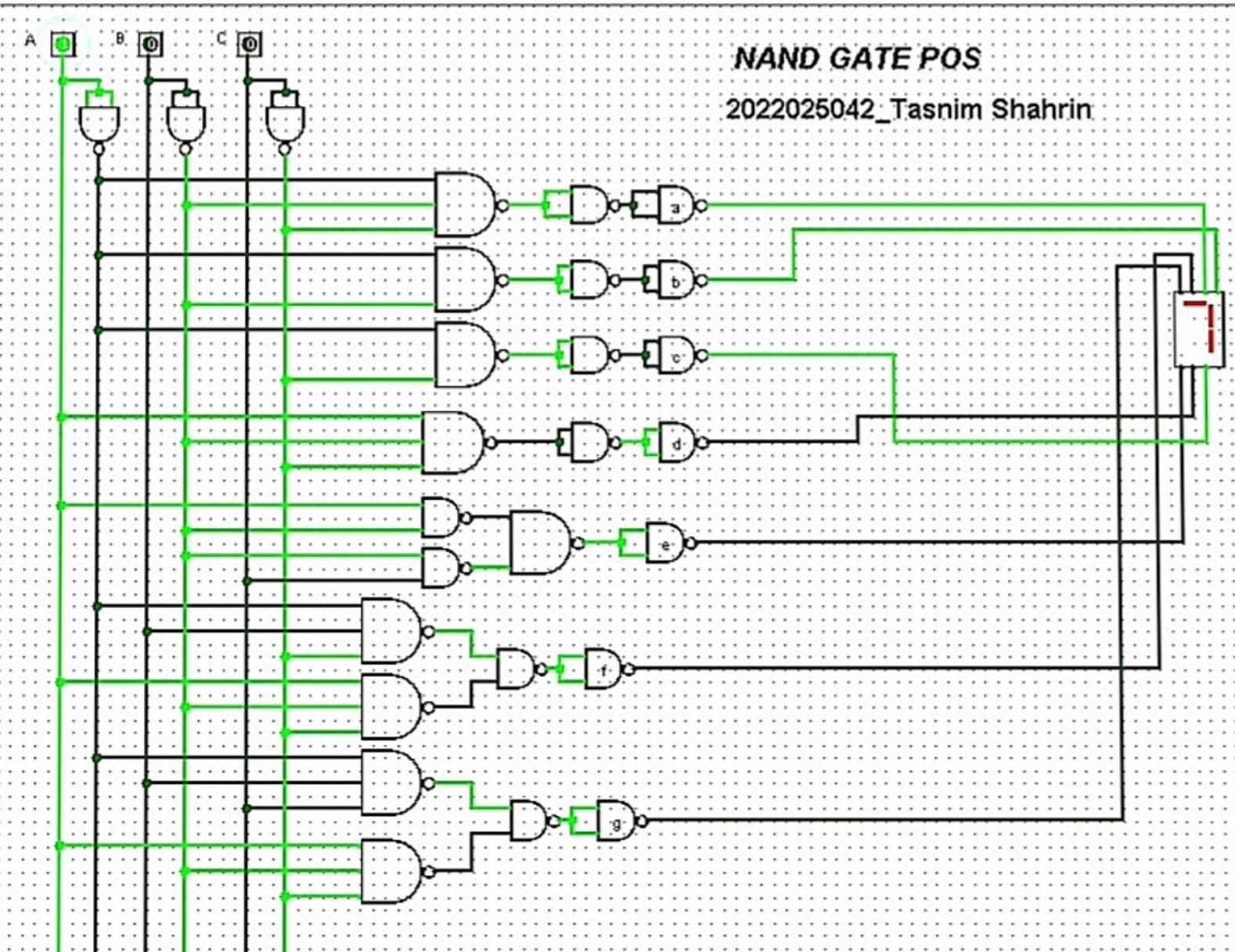


NOR gate POS

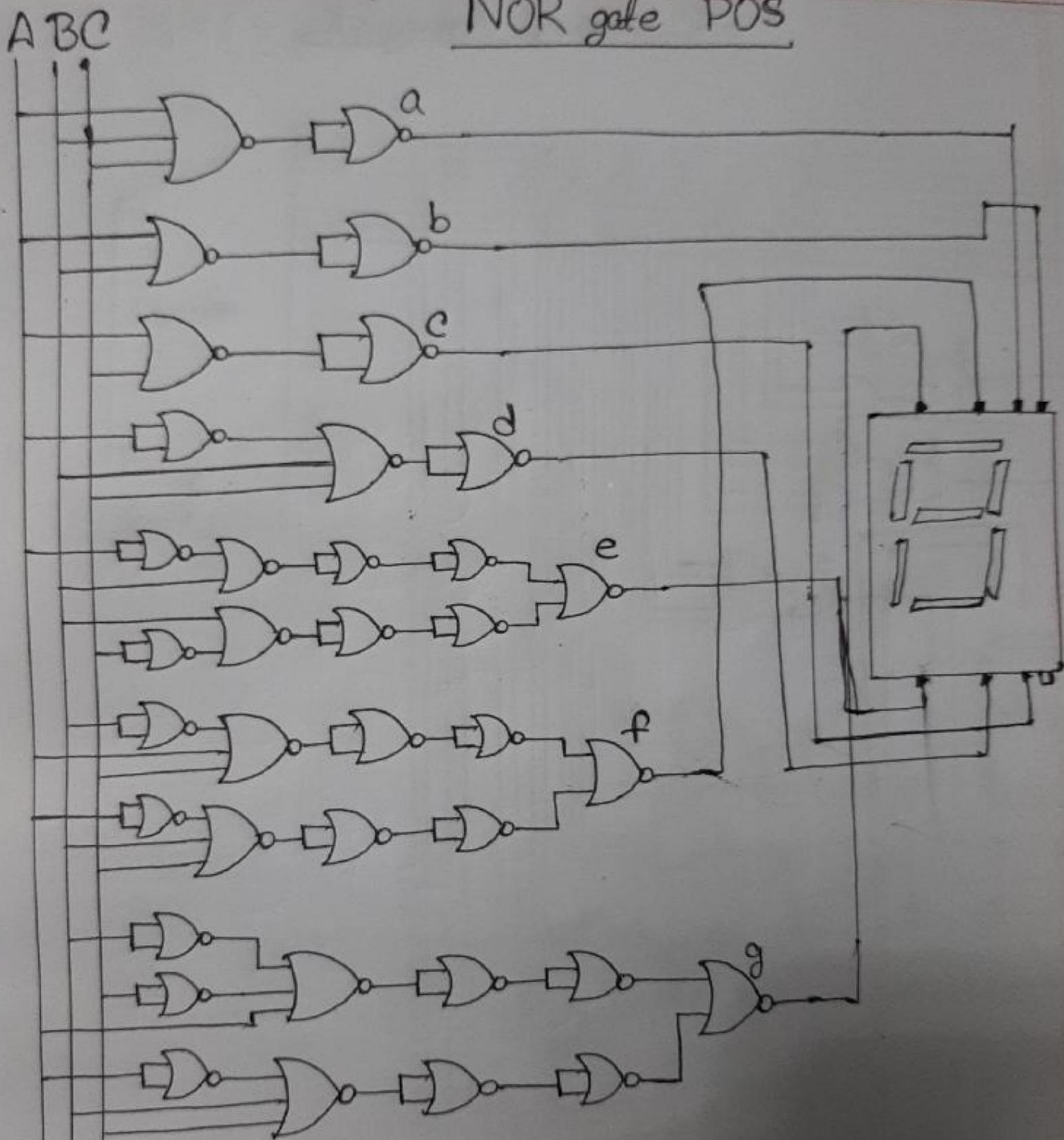


NOR GATE POS


2022025042_Tasnim Shahrin

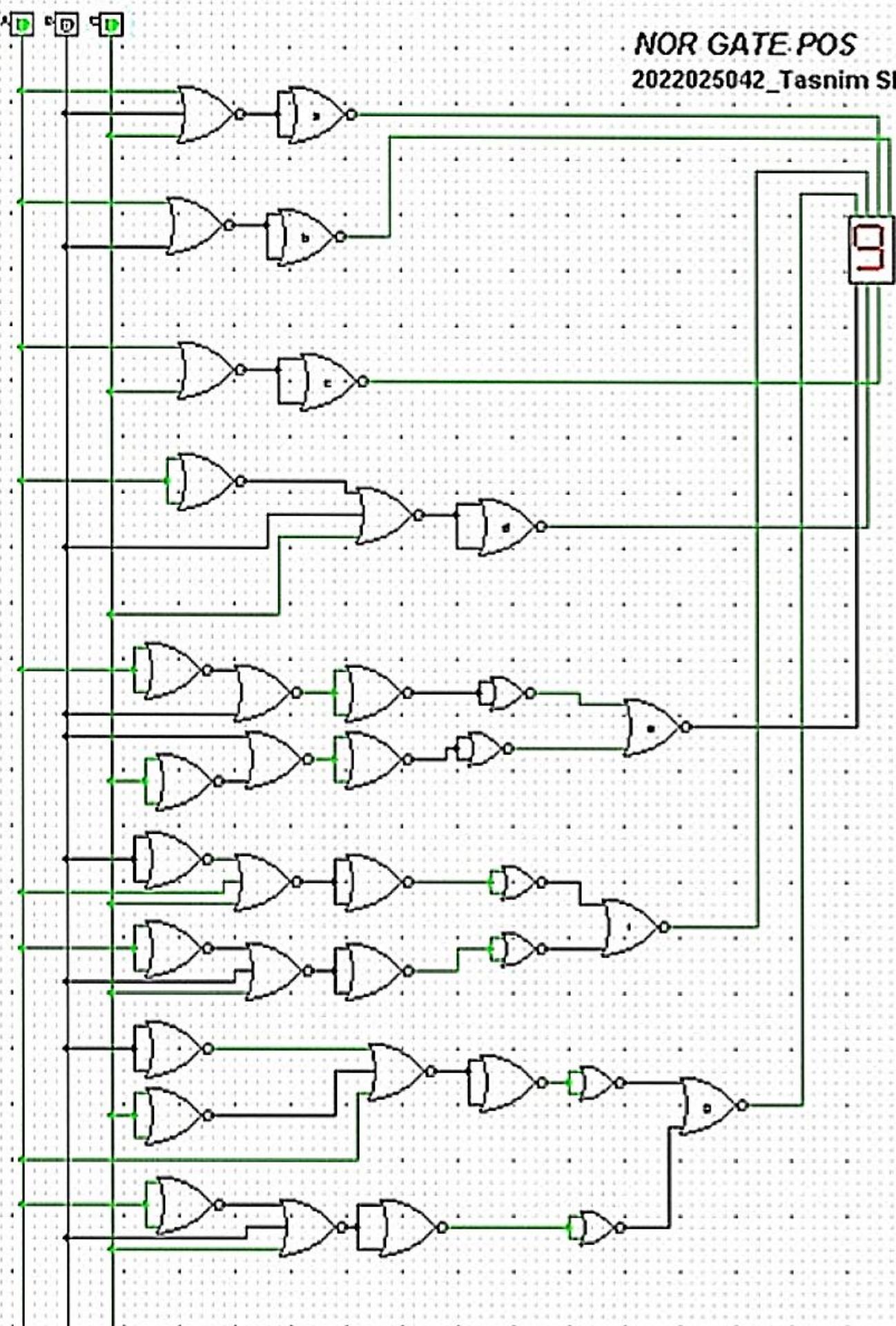



7 Segment Decoder

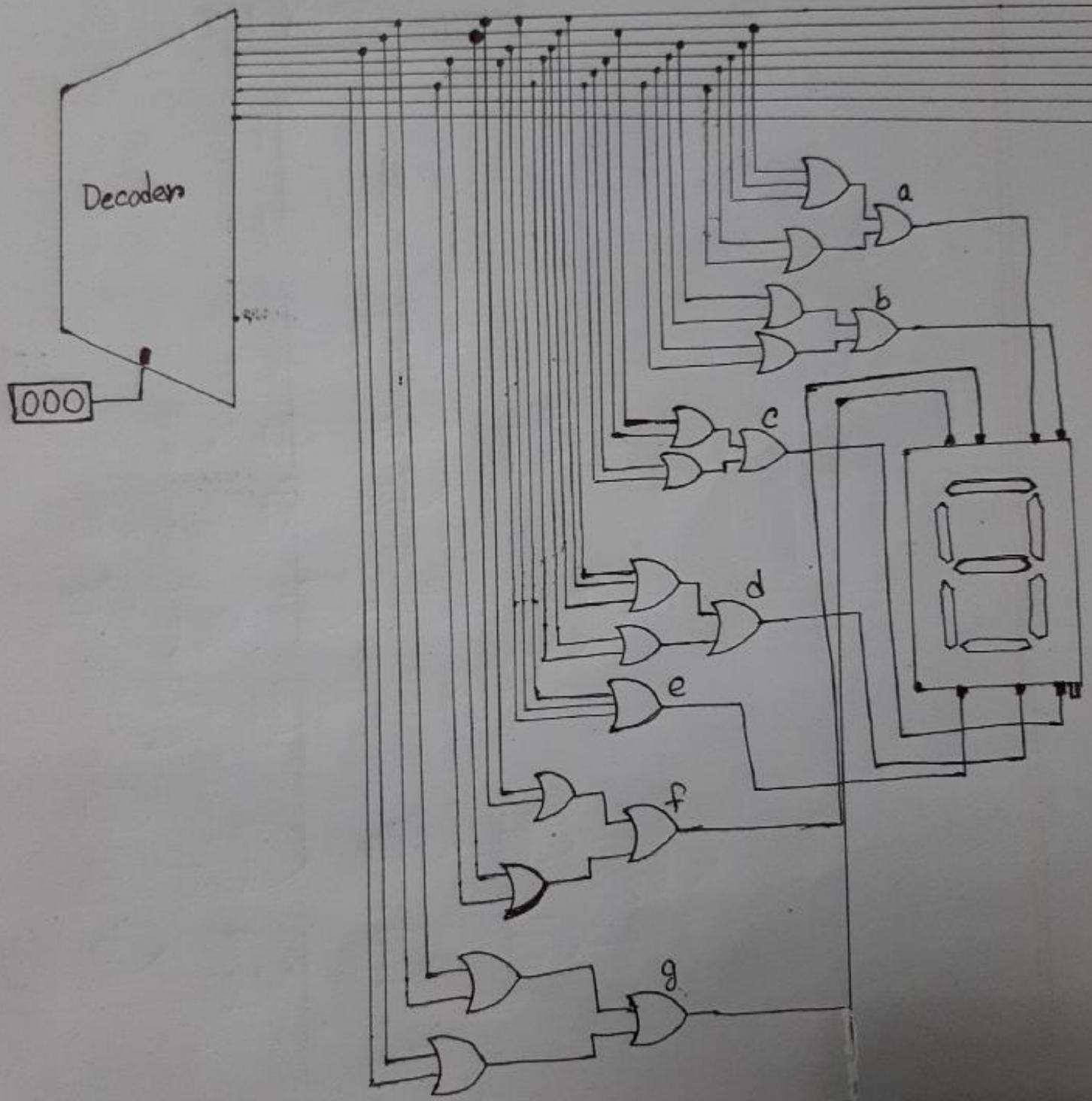

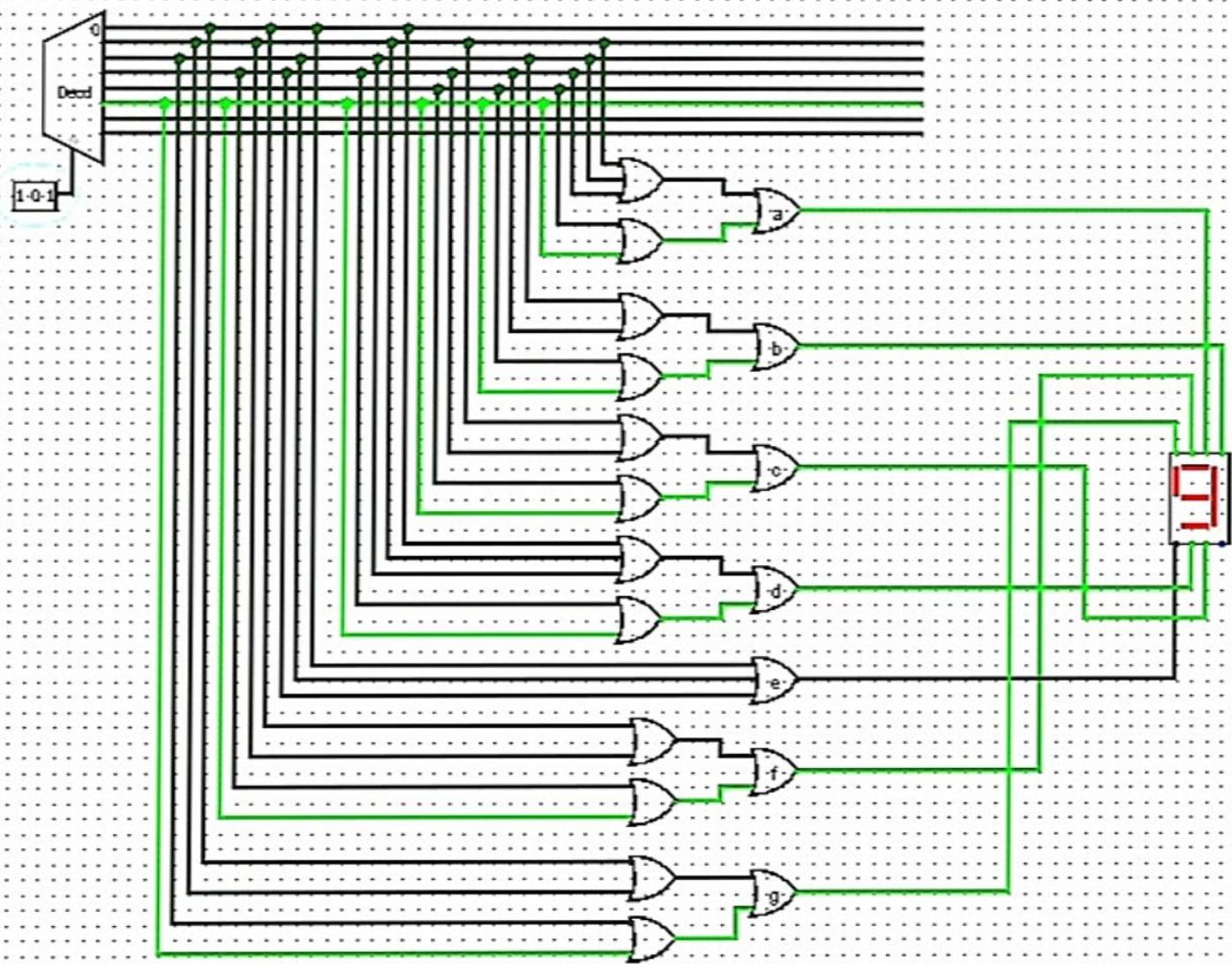7 segment decoder
2022025042_Tasnim Shahrin



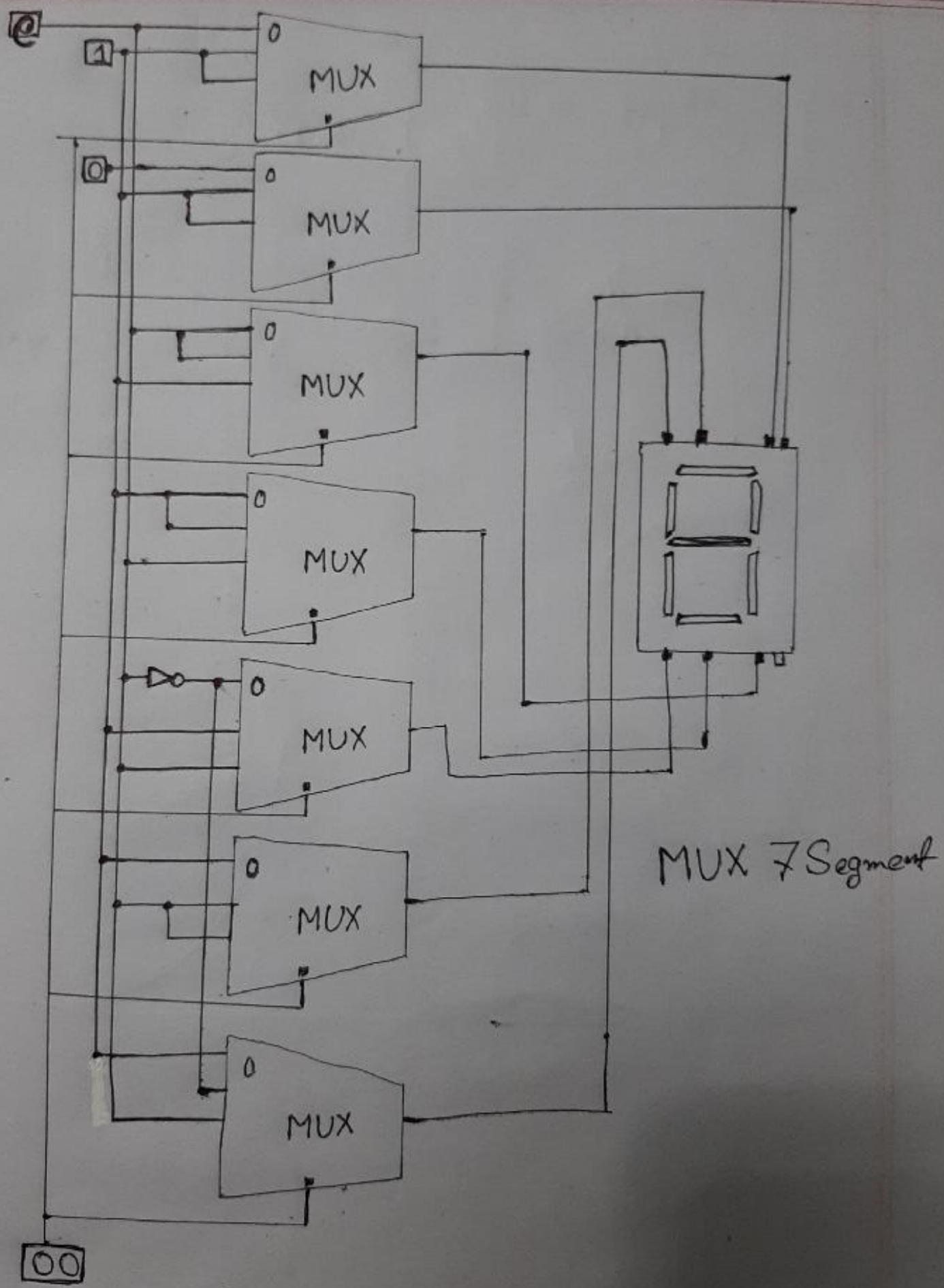

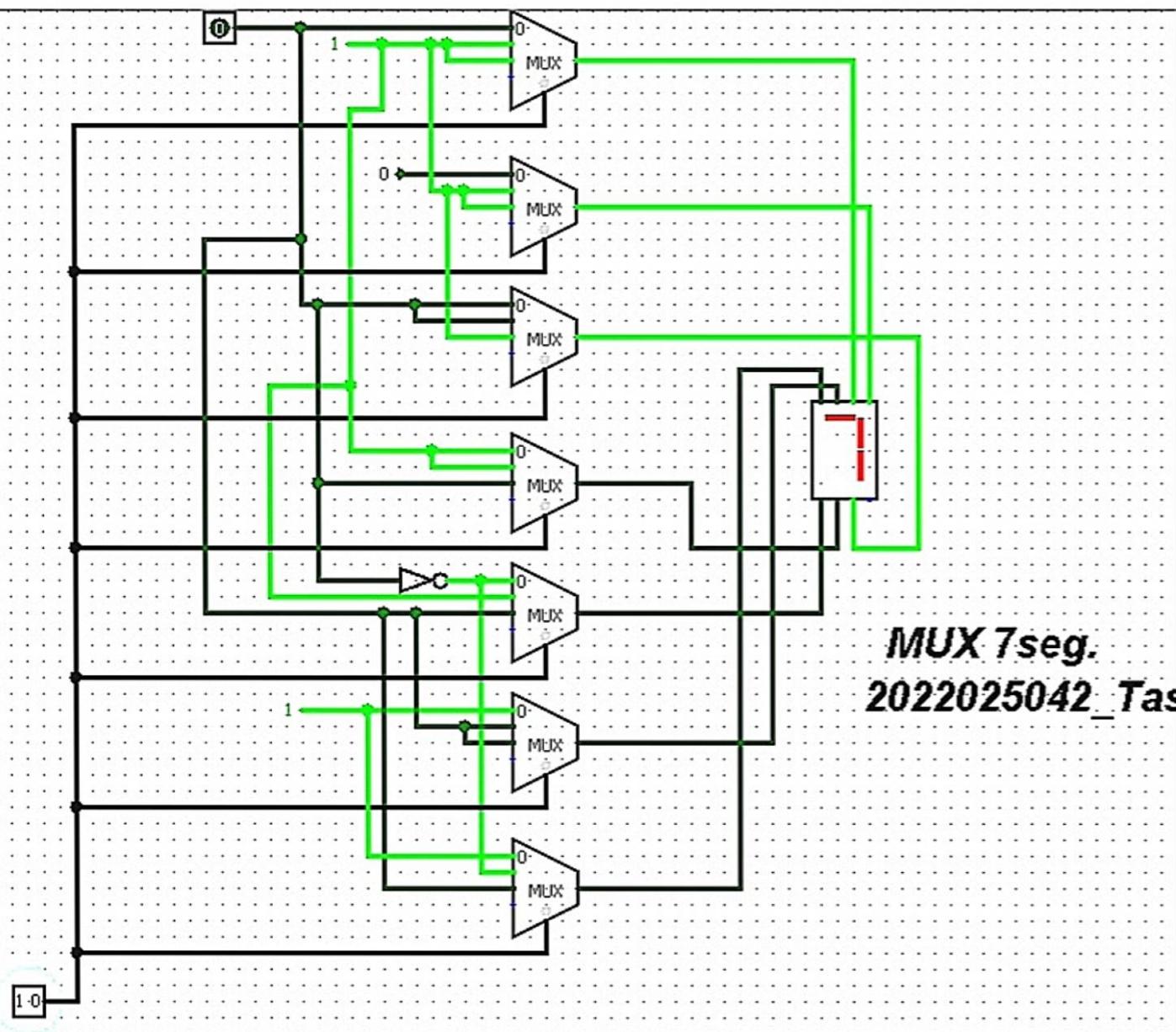

MUX 7seg.
2022025042_Tas

Discussion :

In this project I made 7-segment display to display "7S2079".

At first I made the truth table. By using the truth table I got SOP and POS equations.

I draw the circuits of SOP and POS in the generalized and simplified form.

I also did K-maps for SOP and POS. By the K-maps we got the simplified form. The simplified form is made the circuit quite simple and short.

After that I use the 3 to 8 line decoder, and 4:1 MUX, and use the same truth table to display 7-segment "7S2079".

I also draw and simulate the simplification form of SOP and POS by using NAND and NOR gates.

I draw and simulate the sequential circuit with combinational circuit. I use JK flip-flop to make the input automated.

Typically for a standard red colored 7-segment display, Each LED segment can draw about 15 mA to illuminate correctly, So on a 5V digital logic circuit, the value of the current limiting resistor would be about 200Ω ($5V - 2V$) / 15 or 220Ω to the nearest higher preferred value. So, to understand how the segments of the display are connected to a 220Ω current limiting resistor consider the circuit below.

Conclusion:

This project was good opportunity for all of us to learn how the system works and learn the theory as well. We also faced a lot of problems which taught us what kind of problems can be faced while building a 7-segment display. We had problems mostly with lack of knowledge on how to build everything but with a great deal of time spent on it together we figured it out eventually.